 


# The problem

For any synchronous circuit  $G$ , we define the (minimum feasible) *clock period*.

$$\Phi(G) = \max\{d(p) : w(p) = 0\}$$

$$w(p) = \sum_{i=0}^{k-1} w(e_i) \quad d(p) = \sum_{i=0}^{k-1} d(v_i)$$



# The problem

A *retiming* of a circuit  $G = \langle V, E, d, w \rangle$  is a function  $r : V \mapsto \mathbb{Z}$  that transforms  $G$  into  $G_r = \langle V, E, d, w_r \rangle$ , where

$$w_r(e) = w(e) + r(v) - r(u).$$

